

design Direct Digital Synthesis

FAQs

Don Tuite

Analog/Power Editor

FREQUENTLY ASKED QUESTIONS

How does direct digital synthesis (DDS) work?

There are at least three elements to DDS: a numerically controlled oscillator (NCO) with a phase modulator, a block that converts the phase information to amplitude values, and a digital-to-analog converter (DAC). An in-phase/quadrature (I and Q) modulator may be added ahead of the DAC.

Here's the theory. In a sinusoidal wave in the analog domain, the phase angle of a single frequency, f_a , rotates through a fixed angle at a rate of:

$$\omega \text{ (or } \Delta\text{phase}/\Delta t) = 2\pi f$$

That angular rate of change with respect to time is a linear ramp proportional to the sine wave frequency that returns to zero at the end of each sine wave cycle. In the digital domain, Δt in the expression above becomes the reciprocal of the sample-clock frequency, f_s . This implies that, for any given sample:

$$f_a = (\Delta\text{phase} * f_s) / 2\pi$$

The phase accumulator in the DDS assembles the phase component of the output signal, typically based on a 32-bit frequency-tuning word (FTW) that represents the desired value of Δphase . Clearly, 32 bits provide very fine resolution of the DDS's output frequency. To accomplish phase modulation, a phase offset can be added by means of a separate phase register.

This phase information maps directly into a sequence of amplitude values for the frequency specified by the input word. A block in the DDS then converts that phase information into amplitude values.


Traditionally, sine/cosine lookup tables in memory have accomplished this task. To keep the size of the lookup table manageable, not all of the bits in the FTW are used in the lookup, although they do provide fine resolution in selecting f_a . The output of this block is the input to the DAC, which generates a sequence of amplitudes. A low-pass filter smooths the output of the DAC.

What are the advantages of DDS?

The digital nature of DDS technology provides flexibility, repeatability, and precision. The output is digitally calculated, so it does not deviate over time as long as the reference clock is stable. With careful attention to frequency planning, it also can enhance spurious-free dynamic range (SFDR).

What kinds of applications employ DDS?

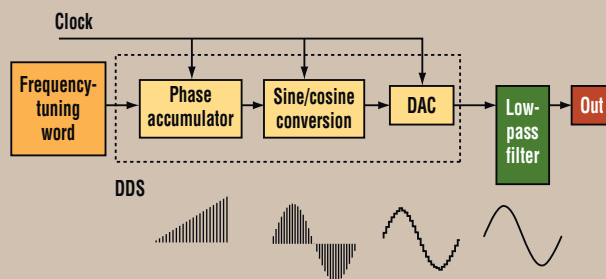Originally, DDS was used to provide tunable local oscillators and signal generators and to implement various modulation



These are the basic functions of direct digital synthesis, with representative waveforms.

schemes. The latest DDS chips are used in those functions as well as in medical imaging, single-side-band suppressed-carrier modulation, phased-array radar and sonar applications, clocking, and acousto-optic tunable filters (AOTFs).

An AOTF is a solid-state electronically tunable spectral-band-pass filter. AOTFs make it possible to extract a single wavelength from multiline or broadband light sources. An RF frequency applied to the AOTF transducer controls the output-light wavelength, while the RF amplitude controls the light's intensity.

What's the history of monolithic DDS chips?

Although DDS technology has been in use since at least the 1970s, it was implemented using separate chips until the mid-1990s. The slowest and most expensive element, the DAC, limited its performance. The first monolithic DDS chips appeared in 1994. They integrated the DAC on the same substrate as the other circuit elements, simplifying implementation and lowering costs.

What's different about the latest DDS chips?

Two- and four-channel chips with guaranteed 72-dB channel-to-channel isolation for two channels and 65 dB for the quad chip are available. They operate from clocks as fast as 500 Msamples/s, producing output frequencies from dc up to 200 MHz in 116-mHz steps. (F_{MAX} is slightly below the Nyquist criterion because harmonics mixed with the clock show up in-band and are too close to be filtered.)

Architecturally, algorithms are replacing lookup tables, providing a more efficient method of converting phase data to amplitudes. A new feature allows synchronous loading of updated amplitude, frequency, and phase information for all channels. The updates take place simultaneously.

Performance-wise, SFDR is higher. The FTW updates more quickly, too. In the fastest new ICs, it updates in 50 ns, which is 32 times faster than in previous chips. For all that, power consumption is lower, down around 165 mW per channel in multichannel DDS chips.

Parts can be programmed for any combination of two-level direct modulation, linear sweep, or single-tone generation without pin constraints. Within certain limits, the simultaneous operation of four-, eight-, and 16-level modulation is possible.

Alternatively, amplitude, frequency, or phase can be modulated. Frequency ramp-up and ramp-down make it possible to increase or decrease the amplitude before and after the modulated data sequence. Linear sweep provides precision stepping of amplitude, frequency, or phase between two points.

What else is new about the latest DDS chips?

Before the advent of multichannel DDS chips, the external delay between ICs made synchronization difficult. Some new dual-channel and quad-channel chips let designers select phase offsets relative to each channel. Improved synchronization techniques can manage applications with more channels.

ED ONLINE 11915

 **ANALOG
DEVICES**


product Q&As

New Multichannel DDS Eases Synchronization Challenges And Reduces Board Space

ADI's new AD9959 (four-channel) and AD9958 (two-channel) multichannel DDS ICs help alleviate design complexity, reduce board space, and offer cost savings, all while achieving high-precision DDS performance.

Inherent Synchronization, Independent Programming

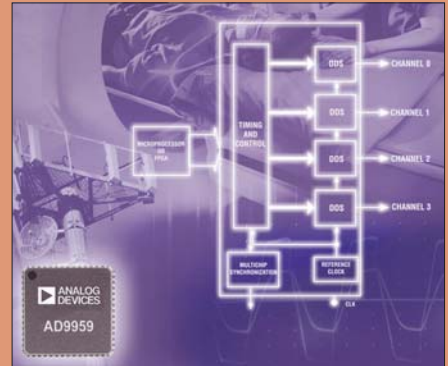Independent programming of up to four inherently synchronized outputs enables designers to achieve precision synchronization between multiple outputs without expending time or effort on this usually complex portion of the system design.



Each fully independent programmable channel provides 14 bits of phase offset tuning, 32-bit frequency resolution, and 10-bit amplitude control. Programmable channel control allows for the correction of imbalances in external signal paths due to analog processing.

Reduce Board Space, Lower Costs

The multichannel DDS ICs simplify the design process by integrating multiple DDS channels on a single chip, eliminating the need for several single-channel DDS chips and external circuitry. This integration reduces board space consumption up to 60% over traditional solutions while lowering system costs.

Both the AD9959 and AD9958 feature:

- Four/two synchronized complete DDS channels at 500 Msamples/s
- Channel-independent phase (14-bit), frequency (32-bit), and amplitude (10-bit) control
- Excellent channel-to-channel isolation
- Greater than 53-dBc wideband SFDR
- Less than 165 mW of power per channel
- Space-saving 56-lead LFCSP

Applications requiring multiple synchronized outputs such as phased-array radar systems, optical communications, automatic test equipment, and medical imaging will benefit greatly.

For more information on the **AD9959 and AD9958 multichannel DDS products**, please visit: www.analog.com/multiDDS



Visit www.digikey.com to get real-time pricing and availability on our wide selection of **Analog Devices** parts!