

White LED Voltage Booster Uses 555 Timer IC

Anthony H. Smith

tony.scitek@tiscali.co.uk

Scitech, Bedfordshire, England


This voltage-booster circuit for driving one or more white LEDs uses a 555 timer as its main element (see the figure). The timer, IC1, functions as a resettable astable multivibrator where R1, R2, and C2 are the timing components.

When the supply voltage, V_S , is first applied, D1 conducts and reservoir capacitor C1 charges to a voltage just less than V_S . Initially, transistor Q2 is off, IC1's RESET input is high, and the OUTPUT pin goes high, allowing C2 to charge up

via R1. During this time, the DISCHARGE pin is pulled up by R4, which turns on Q1, and the current (I_L) in inductor L1 starts to ramp up. Because Q1 is saturated, both D3 and the LED are reverse-biased.

When the voltage on C2 crosses the threshold voltage at pin 6 of IC1, both the OUTPUT and DISCHARGE pins go low, and Q1 turns off. The resulting "back EMF" generated across L1 instantaneously raises the LED's anode voltage (V_A) above V_S , thereby illuminating the LED. Diode D3 is now forward-biased and pulls up IC1's supply voltage ($V+$) to a level some 2 to 4 V higher than V_S .

C2 is now quickly discharged via D2

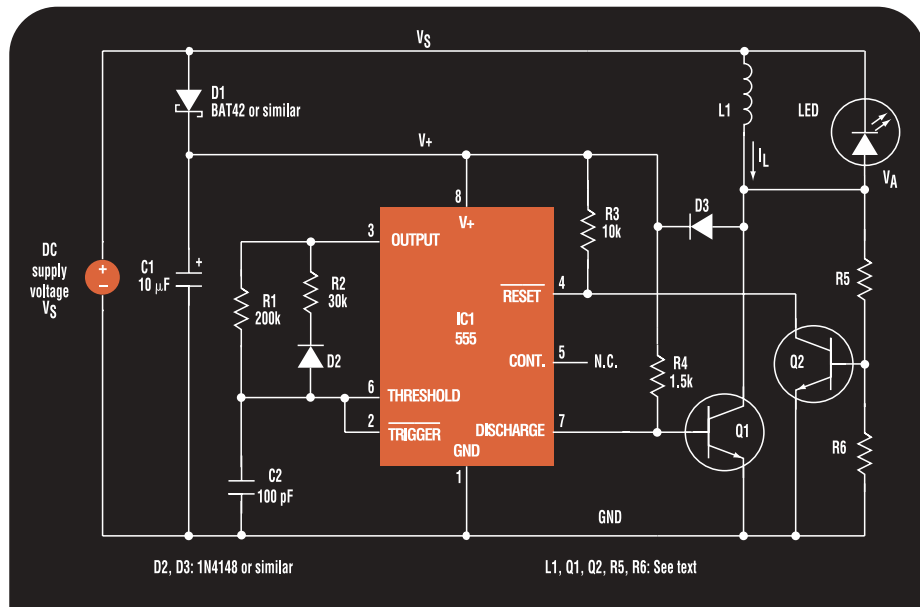

Ideal for single-cell applications, this 555-based boost circuit produces adequate LED intensity even if the supply voltage falls below 1.0 V.



Don Tuite

JUST FOR YOU

Welcome to the first of many "Analog and Power Ideas for Design." The feature will return next month. If the reader response is positive, the plan is to publish this section 13 times in 2005. A&P IFD is the launch of something new and something old for *Electronic Design*.

The magazine has always tried to run as many reader-submitted design articles as possible, but the industry downturn left us strapped for pages until recently. Still, our issue-by-issue reader polls show that you want more design information, and believe me, whenever the *Electronic Design* editors meet, one of the bones of contention is always, "Where's the real design stuff?" We all realize that the real design stuff has to be reader-generated.

The good news is that page counts are rising and *Electronic Design* can now run more design submissions from readers. So, we're returning to something old with a revamped Ideas for Design department.

The new wrinkle is that we're using targeted demographics to deliver additional specialized content to precisely the readers who are most interested in it. In other words, if you're reading this, it's because you indicated an interest in analog or power design when you submitted your subscription form.

Analog and power-supply design are closely tied (try to run a fast, high-res analog-to-digital converter on a noisy rail) and are arguably one of the more mysterious disciplines in the EE curriculum. We hope this section will help all practitioners share the secrets of the craft.

As always, we welcome your comments and suggestions. Send them to me at dtuite@penton.com. ED Online 8977

and R2, ready for the next cycle. Provided the values of R5 and R6 are chosen correctly, Q2 turns on while the LED is $\overline{\text{RESET}}$ input. When the energy stored in L1 is exhausted, the LED and D3 again become reverse-biased, and V_A falls to a low level. Q2 now turns off, allowing IC1 to commence another cycle, and C2 again begins to charge via R1. The process repeats thousands of times a second, so the LED appears to be continually illuminated.

The circuit uses three “tricks” to optimize performance. First, the bootstrapping provided by D3 boosts the timer’s supply voltage, enabling the circuit to continue working even when V_S drops below 1 V. In addition, it provides enhanced base drive for Q1 via R4. Second, the “feedback” provided via Q2 ensures that a new cycle begins as soon as L1’s energy is depleted, thereby maximizing the average LED current. Third, Q1 is driven from the timer’s open-drain DISCHARGE terminal, rather than from the OUTPUT pin. Therefore, the base drive doesn’t depend on the current-source capabilities of the 555’s output terminal.

Transistor Q1, which should be a low-saturation type, is driven on for a time t_{ON} , given by:

$$t_{ON} = K \times R1 \times C2 \quad (s)$$

where K is a constant that depends on the particular type of 555 timer used. The LED’s peak current is roughly equal to the maximum inductor current, $I_{L(max)}$, where:

$$I_{L(max)} = [(V_S - V_{CE(sat)})/L1] \times t_{ON} \quad (A)$$

If Q1’s saturation voltage is low, say less than 50 mV, we can ignore $V_{CE(sat)}$ and simplify the expression to:

$$I_{L(max)} = (V_S/L1) \times t_{ON} \quad (A)$$

Thus, for a particular value of V_S , the values of R1, C2, and L1 may be selected to obtain the largest value of $I_{L(max)}$ that produces maximum LED brightness without exceeding its peak current rating.

Resistors R5 and R6 should be chosen to ensure that Q2 is off when $V_A = V_S$ (the case when power is first applied), and on when the LED is forward-biased ($V_A > V_S$). Q2 itself should be a small-signal device with good current gain.

For efficient, low-voltage operation, a CMOS timer such as Intersil’s ICM7555 or Texas Instruments’ TLC555 should be used. These types are specified to function with a supply voltage as low as 2.0 V.

Plus, their internal discharge transistors are able to pull pin 7 down to around 100 mV or less, ensuring that Q1 can be turned fully off.

A test circuit built using a TLC555 for IC1, and Q1 = ZTX649, Q2 = BC546, L1 = 100 μ H, R5 = 56 k Ω , and R6 = 10 k Ω was found to start up with V_S as low as 1.0 V. The circuit produced excellent brightness in a Lumileds (www.lumileds.com) LXHL-PW01 white LED. Transistor Q1’s “on” time (t_{ON}) was around 20 μ s, resulting in a peak inductor current of around 300 mA at $V_S = 1.5$ V. However, this could easily be altered by changing the values of C2 and R1, and/or L1. Performance was equally impressive using an ICM7555, although the minimum startup voltage was slightly higher at 1.2 V.

The circuit is ideal for single-cell applications, because it continues to generate adequate LED intensity even when the supply voltage falls below 1.0 V. Also, two or more LEDs may be connected in series, although there will be a corresponding reduction in brightness. **ED Online 8968**

ANTHONY H. SMITH, consultant engineer, received a BSc (Hon) in electronics from Salford University, Greater Manchester, U.K.

Handy Circuit Options Boost Output Of Capacitive Supplies

Louis Vlemincq

louis.vlemincq@belgacom.be

Belgacom, Evere, Belgium

Capacitive supplies are very attractive for applications that don’t require isolation from the mains supply. Simple, inexpensive, lightweight, and reliable, they run cool and don’t generate interference. However, they suffer from a significant disadvantage: If you need an output current in excess of tens of milliamperes, the dropping capacitor tends to become bulky. This is especially true when the output must be referenced to one of the mains terminals, as is often the case with triac-driving circuitry. The only option then is to use the half-wave voltage-doubler topology, which unfortunately halves the available output current.


Another solution is to use a current-multiplying rectifier to boost the output current. By adding some components to the standard half-wave doubler circuit (*Fig. 1a*), you obtain the current-doubling variant (*Fig. 1b*).

In Figure 1b, another capacitor (C3) is inserted into the path of the positive half-cycle current. Thus, it receives the same charge as C2, the main output capacitor.

During the negative half-cycle, D3 is blocked while Q1 conducts via R2, connecting the positive side of C3 to that of C2. On the negative side, D1 provides a path from C3 to the ground, which effectively parallels both capacitors. This doubles the charge that’s transferred each cycle to the output, also doubling the available output current. D4 resets the charge of C1 during the negative half-cycles. With this improvement, we’re now on an

Tiny, yet powerful MOSFET gate drivers

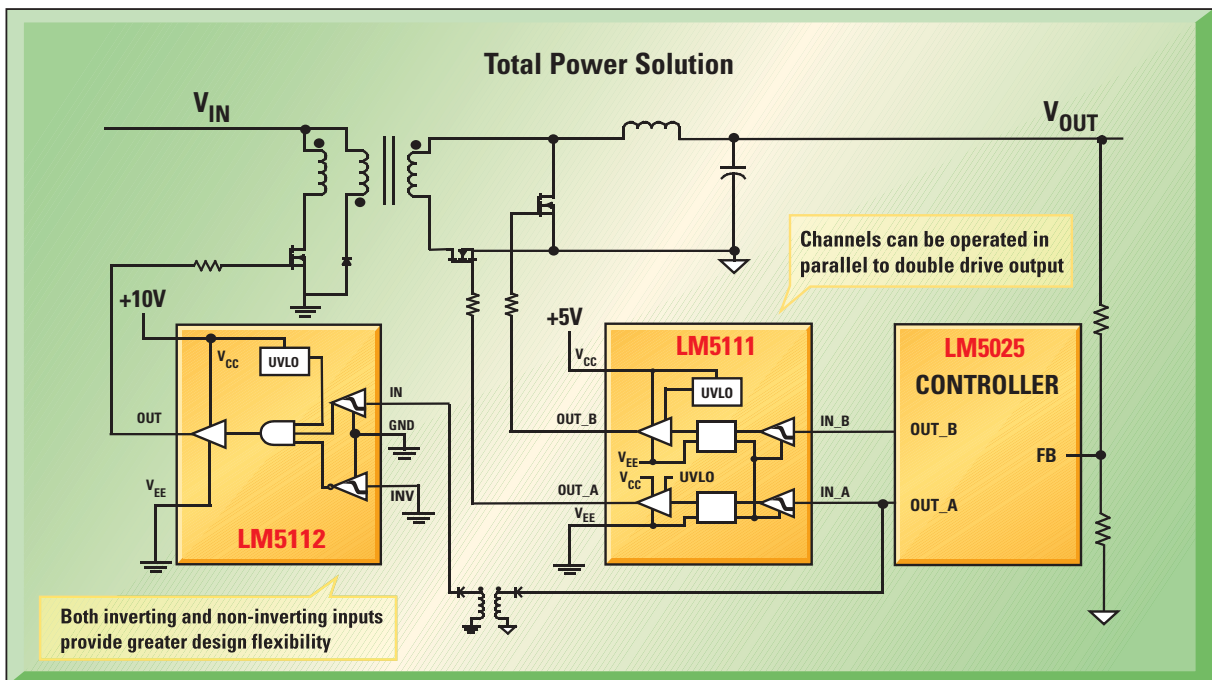New LM5111 dual 5A peak and LM5112 single 7A peak for high-peak gate drive current



Features:

- High-current drivers provide faster switching times and improved efficiency in high-frequency applications
- “Compound” output driver stage includes MOS and bipolar transistors operating in parallel
- Reduced drive current variation with supply voltage and temperature
- Wide 3.5V to 14V operating supply voltage range
- Built-in under-voltage lockout (UVLO) protection
- LM5112 capable of sinking more than 7A peak from capacitive loads
- Available in SOIC-8 (LM5111) and tiny, thermally enhanced (<math><50^{\circ}/W</math>) LLP-6 (LM5112) packaging

Ideal for use in high-frequency modular DC-DC power converters where PCB size and efficiency are a premium





For samples, evaluation boards,
datasheets, and online analog courses,
visit us today at: power.national.com

Or call: 1-800-272-9959

 **National
Semiconductor**
The Sight & Sound of Information

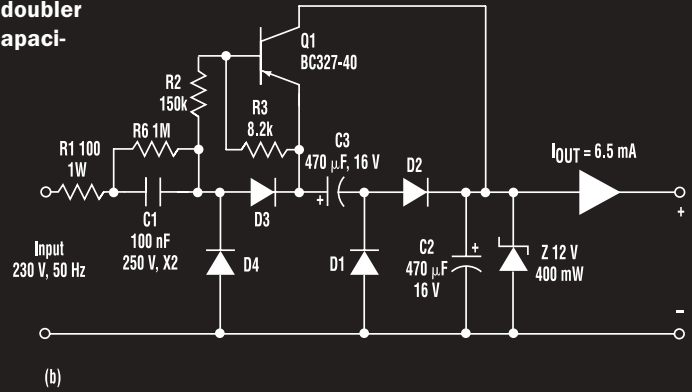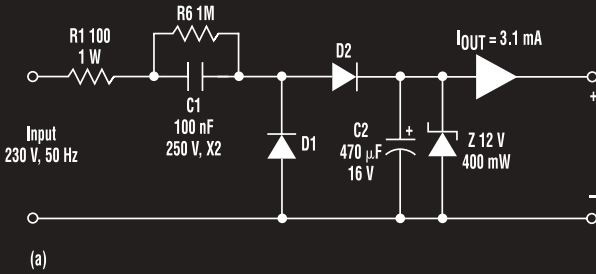1. By adding some components to the standard half-wave doubler circuit (a), it's possible to double the output current of a capacitive supply (b).



equal footing with a full-wave circuit, but with a common terminal between the input and the output.


Further improvements are also possible. Up to this point, the negative half-cycle hasn't actively contributed to the current output. The circuit of Figure 2 changes that situation. During the negative half-cycle, C4 is charged via D5 and D7, and Q2 is blocked because it's negatively biased. When the input becomes positive, Q2 conducts via R4, as does D6, connecting C4 to the input of the previously examined circuit. This effectively doubles its input current. Because it operates "blindly" on any current, whatever its origin, it also gets doubled. The end result is an output current equal to four times that of the initial circuit of Figure 1a.

It's worth saying a word about component selection, especially for those unfamiliar with capacitive supplies. For safety reasons, it's essential that C1 be an X-rated model (that is, suitable for connection across the mains). A 100-nF value was used in this example. The value of R1 isn't critical. It simply limits the inrush current when the supply is plugged in and the ac waveform is at or near its maximum. But it should be able to withstand the full mains peak voltage, which is 325 V in the example.

But it's better to plan for the worst case. If the circuit is plugged in carelessly, the capacitor may be charged to a maximum, then disconnected briefly and connected again to the mains waveform at the opposite maximum. If this happens, the peak voltage seen by the resistor is twice the mains peak voltage, or 650 V in this example. If a 100- Ω resistor is used, as in the example, the peak current will exceed 6 A. Although this peak is of a short duration, it heavily stresses the resistor.

Therefore, you should either select a component specifically

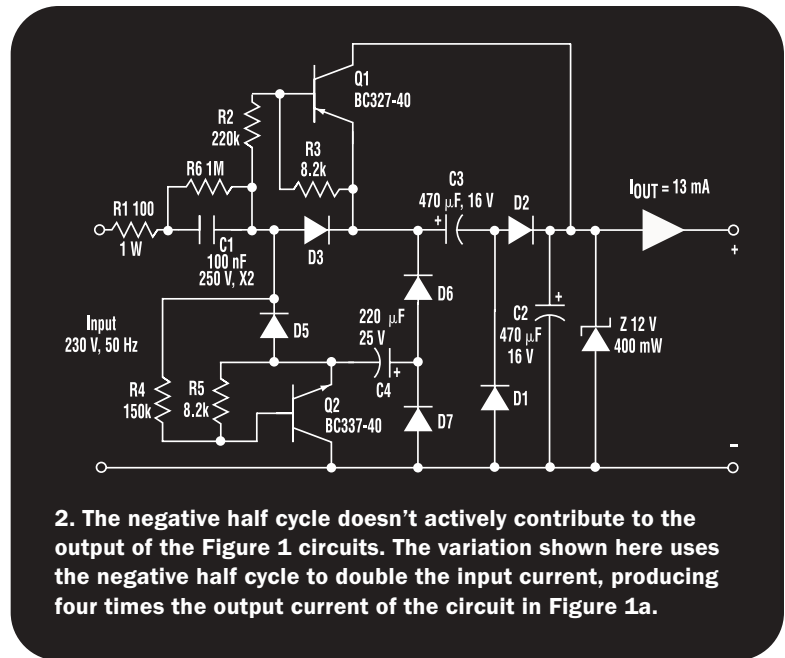WARNING: As with all capacitive supplies, a potentially lethal shock hazard exists because the output is galvanically connected to the mains. Be sure to observe the correct power-line polarity. An isolation transformer is recommended when working on, or testing, the circuit. Make sure that all local electrical codes are followed.



2. The negative half cycle doesn't actively contribute to the output of the Figure 1 circuits. The variation shown here uses the negative half cycle to double the input current, producing four times the output current of the circuit in Figure 1a.


designed for pulse operation or use an oversize standard resistor. A 1-W standard film resistor appears to work well with up to 1- μ F capacitors. Then, if the resistor is too small and eventually fails, the good news is that it will fail open-circuit. Carbon-composition resistors have almost completely disappeared nowadays, and they should never be used in this application because of their propensity to fail in unpredictable ways, posing a serious fire hazard.

R6 is optional. It's a discharge resistor preventing the continued presence of a high voltage on the mains plug terminals after the equipment is unplugged. Although the energy stored in C1 isn't high enough to be harmful, it can give an unpleasant shock to the user. C2, the filter capacitor, should be dimensioned according to your ripple requirements (not forgetting that the ripple frequency equals the mains frequency). C3 is identical to C2. The value of C4 is half that of C2, but it sees a double voltage.

SIMPLIFY POWER SUPPLY DESIGN AND REDUCE BOARD SPACE BY UP TO 59%

iP1201 and iP1202 Two-Phase DC-DC Power Blocks from International Rectifier

iP1201 iP1202

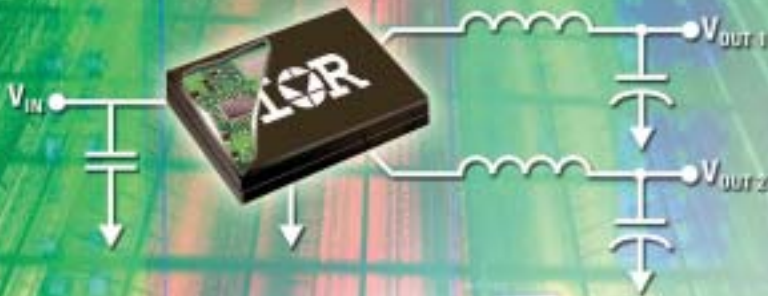

Part Number	iP1201	iP1202
Package	BGA 9.25mm x 15.5mm x 2.6mm	BGA 9.25mm x 15.5mm x 2.6mm
V_{IN} (min/max)	3.14V - 5.5V	5.5V - 13.2V
V_{OUT}	0.8V-2.5V for 3.3V _{IN} 0.8V-3.3V for 5V _{IN}	0.8V-5V for 12V _{IN} 0.8V-3.3V for <6V _{IN}
I_{OUT} - Double sided heatsinking*	15A dual 30A single	15A dual 30A single
I_{OUT} - Single sided heatsinking**	11.5A dual 23A single	11A dual 22A single
Frequency	200 - 400 kHz	200 - 400 kHz

Conditions

*Case & PCB temperature regulated to 90° C

**PCB temperature regulated to 90° C, no airflow

Networking and telecommunications designers now have a simple solution to complex power conversion with the iP1201 and iP1202 **iPOWER™** building blocks from International Rectifier.

Fully optimized for medium current synchronous buck applications, the extremely flexible iP1201 and iP1202 supply two independent voltage rails, or a two-phase output for a single voltage rail for a wide input and output voltage range.

Features

- Full-function PWM control
- No de-rating requirements up to 90°C
- Over-voltage and over-temperature protection
- Interleaved Bi-phase operation
- Configurable as a single two-phase output, or two independent outputs

IR Advantage

- Benchmark power MOSFET chipsets matched with feature rich IC in thermally enhanced BGA package
- Up to 88% efficiency at full rated load current
- Guaranteed low power loss
- Requires fewer external components, replacing up to 20 discrete devices
- Web-enabled SPICE circuit simulation (mypower.irf.com)

Take your simpler and smaller synchronous buck designs to market faster using new **iPOWER** building block solutions from International Rectifier, the power management leader.

for more information call 1.800.981.8699 or visit us at

<http://ipowir.irf.com/ip120x>

READER SERVICE 95

International
IR Rectifier

THE POWER MANAGEMENT LEADER

hfc shorts

Continued

The peak current ratings for Q2 and Q1, respectively, are the output current and twice that value. Their base resistors must be computed accordingly. The diodes aren't critical, but they should not be underdimensioned, due to the aforementioned turn-on peak current. The 1N4001 diodes are perfectly suitable.

This circuit reduces size at the expense of some complexity. The cost is on average similar to that of the standard solution, being rather lower for high currents and

vice versa. Although the circuit is fairly reliable, it can't match a plain capacitor in this respect: Each component added also increases the risk of failure. Therefore, if you're looking for the highest possible reliability, the conventional solution of Figure 1a remains preferable. **ED Online 8969**

LOUIS VLEMINCO, transmission specialist at Belgacom, obtained a master's degree in electronics from the InRaCi (Institut de Radio-Cinematographie), Forest, Belgium.

products

Bridge-Power Supplies Pack 22 2700-F Ultracaps

Bridge-power units for telcos, data centers, and hospitals supply power for the brief interval between failure of the mains supply and the time that full backup power is available from fuel cells or generators.



Traditionally, these have been flywheel-based. But a pair of new products from Maxwell Technologies stores energy in 22 2700-F ultracapacitors. This is Maxwell's first system-level product, complete with ultracapacitors, a dc-dc boost converter, dc charging circuit, cell balancing, and status indicators. The company's 1.6- and 2.3-kW PowerCache products provide 48-V power during startup or transfer to generators, microturbines, fuel cells, or other alternative primary or backup energy sources. Pricing is \$7500 for single units. Contact the company for large-volume and OEM sales. **ED Online 8970**
Maxwell Technologies
www.maxwell.com


Module Enables Energy-Efficient Switching Power Supplies

The LNK302 from Power Integrations is an alternative to capacitive droppers and linear transformers in home appliance and industrial control applications. Like other members of the LinkSwitch TN family, the LNK302 lets designers create energy-efficient switching power supplies in buck or buck-boost configurations and with universal input (85 to 265 V ac) and $\pm 10\%$ load regulation. Other integrated features include a 700-V Power MOSFET, an oscillator with simple on/off control, high-voltage startup, current limit, and hysteretic thermal shutdown circuitry. A 66-kHz switching frequency automatically skips cycles at light load to conserve energy, while frequency jittering minimizes electromagnetic interference. Unit pricing in 1000-piece quantities is \$0.49. **ED Online 8971**
Power Integrations
www.powerint.com



Parallel LED Driver Hits 93% Peak Efficiency

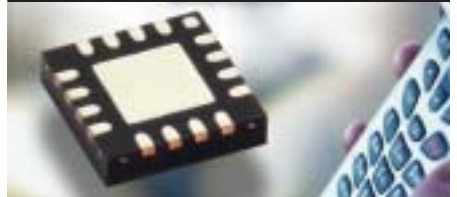The FAN5607 constant-current parallel LED driver from Fairchild Semiconductor provides analog and/or pulse-width-modulation brightness control for LCD backlighting in ultra-portable applications. It




uses a three-mode charge pump and achieves 93% peak efficiency. Internal auto-sense circuitry maintains high efficiency, even when driving less than a maximum of four LEDs, and ensures very tight current matching over the full range of LED current. Also, it requires no external control signal to maintain efficiency when driving fewer than four LEDs. It comes in a 4- by 4-mm molded leadless package (MLP). Thousand-unit pricing is \$0.90 each. **ED Online 8972**

Fairchild Semiconductor
www.fairchildsemi.com

Converters Reach 1000-W/in.³ Densities And 95% Efficiency

The NAT and NAS series of 12- and 20-A converters from NetPower Technologies achieve power densities up to 1000 W/in.³ with up to 95% efficiency. The NAT (in a single-inline package form factor) and NAS (in a surface-mount form factor) are available in two input voltage ranges: 2.4 to 5.5 V and 8 to 18 V. Output voltages range from 0.8 to 8 V. A baseplate option allows conduction cooling. The NAS and NAT devices are priced from \$11.50 for 12-A converters and from \$15 for 20-A converters, both in quantities of 1000. **ED Online 8973**
NetPower Technologies
www.netpowercorp.com

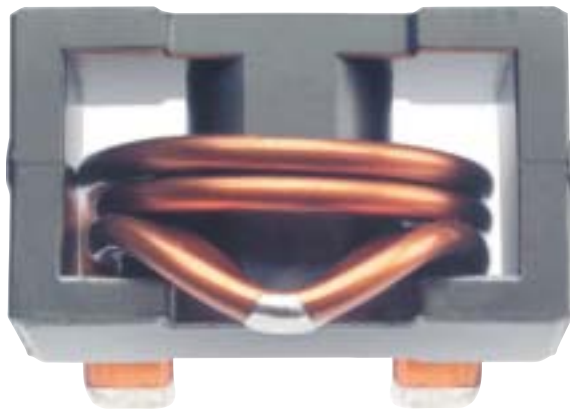Our new 100 Amp power inductors should make everyone smile



Especially if you're working on low voltage, high current power applications!

Our new SER Series inductors are available with ratings up to 100 Amps (*actually, they aren't even close to saturation at that current*) which lets you maximize your current per phase. DC resistance is low and tight, with less than 5% tolerance. The cores exhibit no thermal aging. And their flat wire, self-lead construction assures maximum density, reliability and heat transfer.

Coilcraft's SER Series inductors are available with L values from 0.3 to 10 μH . Or we'll design a part for your specific L and current requirements.

For complete specifications, SPICE models and free evaluation samples of all our new SER inductors, visit us at www.coilcraft.com/ser3



SER2000 Series
Inductance: 0.3 - 2 μH
I sat up to 100 A
Designer's Kit C174 \$60

SER1590 Series
Inductance: 0.3 - 1 μH
I sat up to 50 A
Designer's Kit C166 \$60

SER1360 Series
Inductance: 0.33 - 10 μH
I sat up to 40 A
Designer's Kit C165 \$65



ORDER DIRECT
800-322-2645
OVERNIGHT DELIVERY! CALL BY 5 CST.

Coilcraft

www.coilcraft.com 800/322-2645